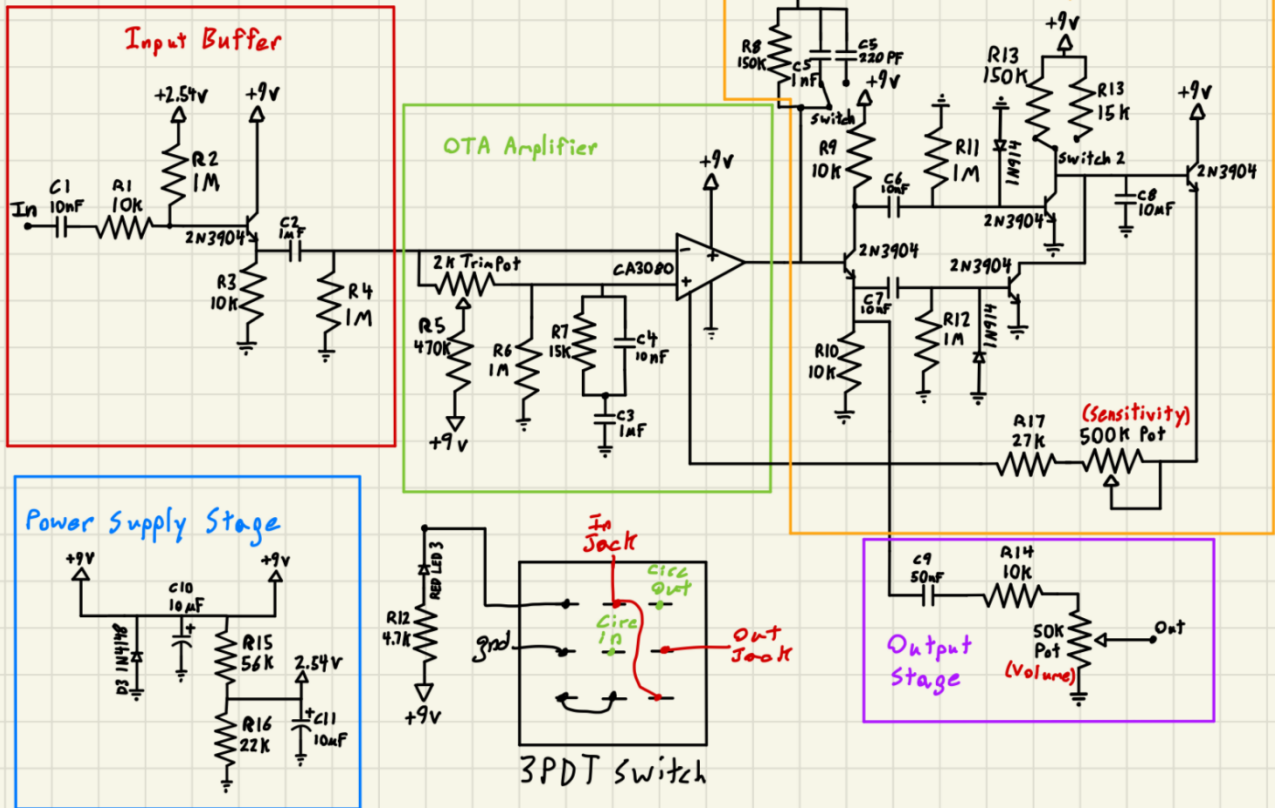


# Dyna Comp Circuit found on Electrosynth



Parts:  
 2N3904x5  
 1N4148  
 1N914x2  
 10nFx4  
 10kx5  
 1Mx5  
 1mFx2  
 trim Pot 2k  
 470k  
 15k  
 1nF  
 150kx2  
 10uFx3  
 27k  
 50pF  
 22k  
 56k

Figure 1: Circuit notes.

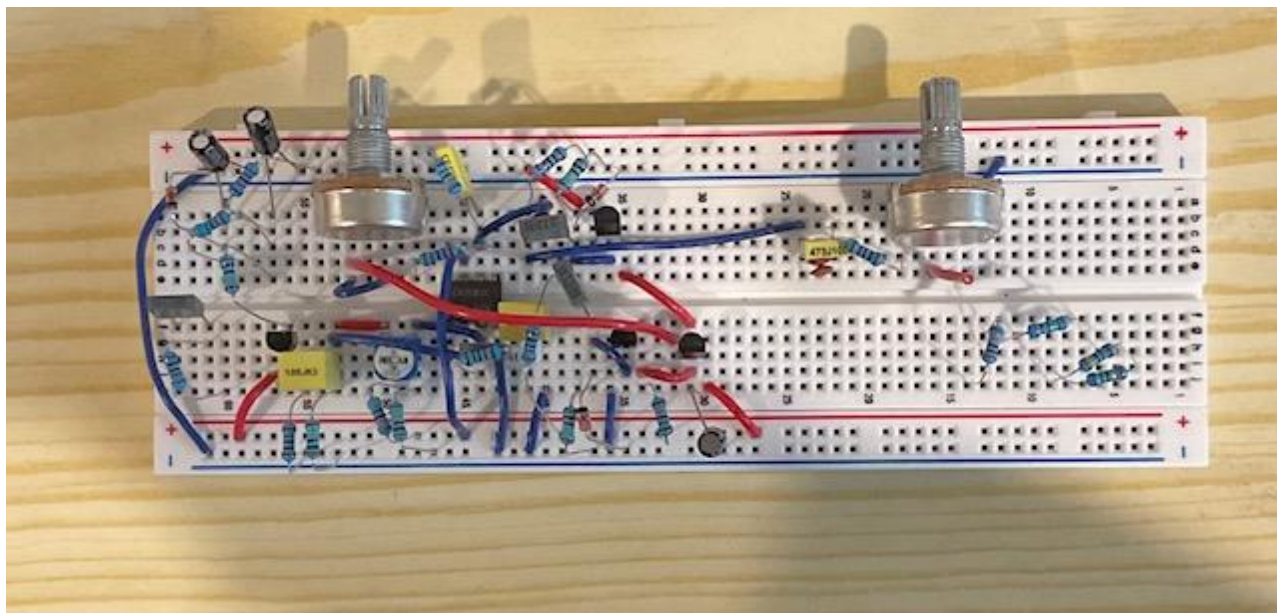


Figure 2: Prototype Circuit on Breadboard.



Figure 3: Completed PCB (Front).

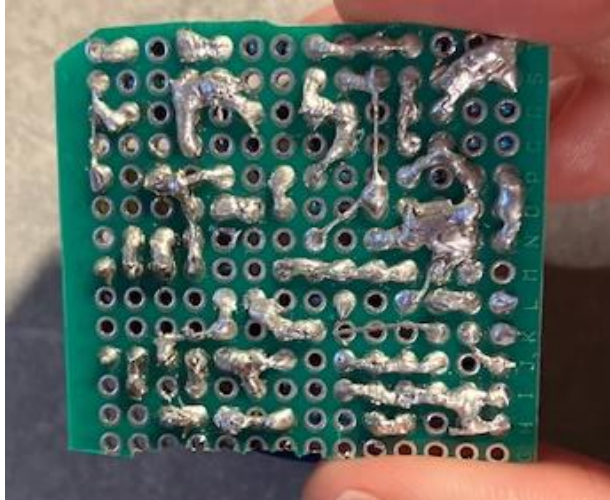


Figure 4: Completed PCB (Back).


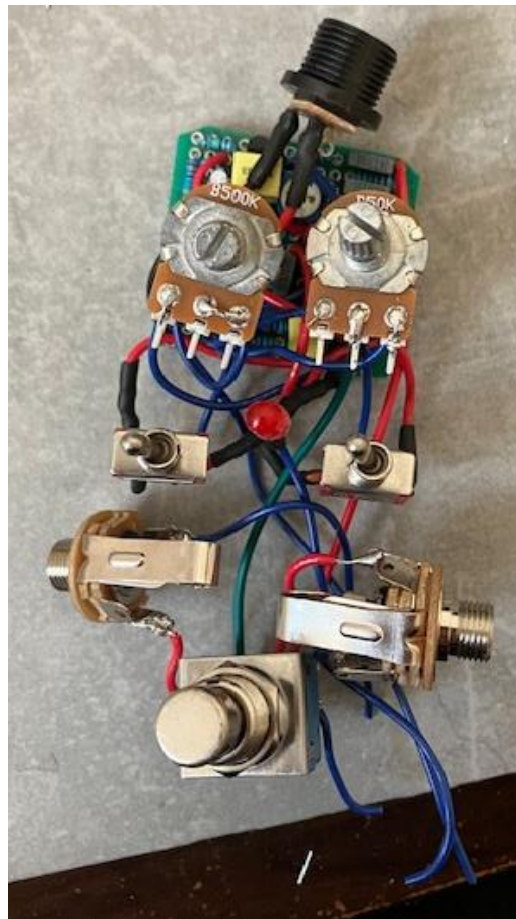


Figure 5: Connected Electronics (Top View).

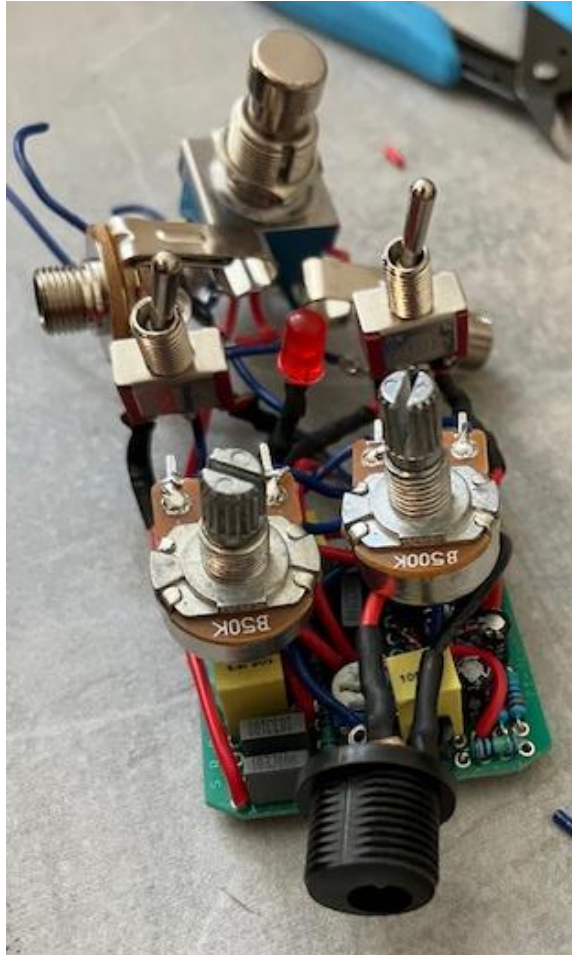



*Figure 6: Connected Electronics (Front View).*



*Figure 7: Connected Electronics (Side View).*

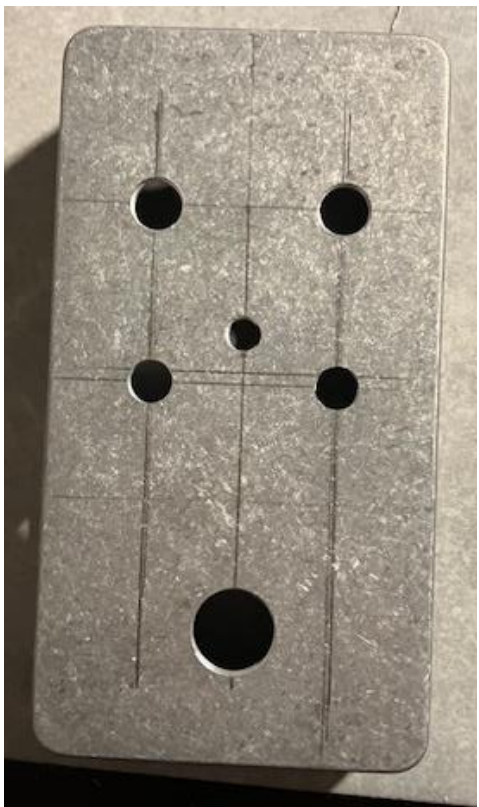


Figure 8: Enclosure measured and drilled.



Figure 9: Electronics assembled in the enclosure.



Figure 10: Final Design.